


A night scene featuring a vibrant display of fireworks in shades of red, orange, and white against a dark sky. In the foreground, several bright green laser beams crisscross the scene, originating from a structure on the left. The bottom of the image shows silhouettes of people and structures, suggesting a public event or festival.

# A 24 GHz beacon source using IQ upconversion

Andy Talbot G4JNT
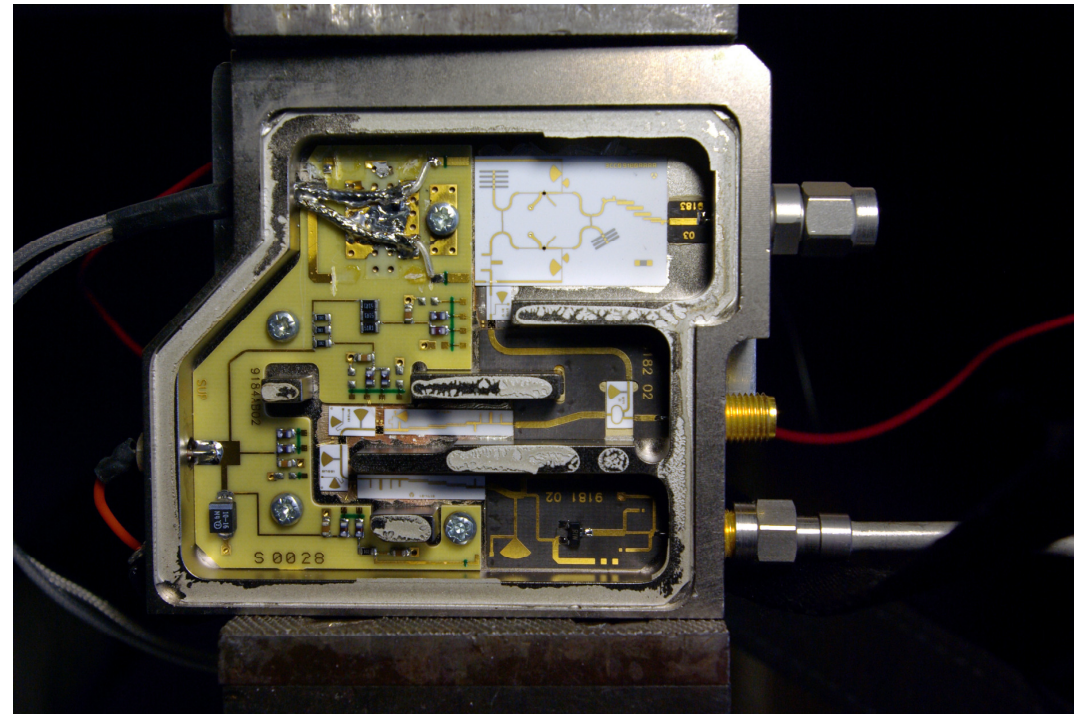
# White Box Modules

- Drive is LO/2 to a pair of Subharmonic mixers
  - Internal Doubler for drive at 6GHz
- Quadrature image cancelling mixer at 24GHz
- 90° Hybrid at ~700MHz
- Remove the hybrid and go direct to diodes



# A Very Simple Solution

- DC Through diodes just controls level
- ON-OFF with ramping
- Wasteful, throws away the image cancelling capability

# Baseband upconvert

- Direct Baseband drive to diodes, I/Q folded spectrum
  - (third method SSB generation)
- Quadrature audio DDS, analogue allpass OPAMps, or DSPIC
- OPAMPs need to present a  $50\Omega$  source, but only have to supply  $<1.5V$  pk-pk drive. So NE553x opamps and resistors work FB.
  
- Need to generate exact centre frequency for LO


# Frequency Setting


- No scope for fiddling with centre frequency using Direct U/C.
- So we must use a Fract-N synth or sit on a wide spaced grid
  - Fract-N at 24GHz is potentially going to be a bit noisy and spurious-ridden
  - And has to generate at 6GHz
- ADF5355 is an off the shelf solution, but as I only had one of those and didn't want to dedicate it to a beacon, what other options were there?




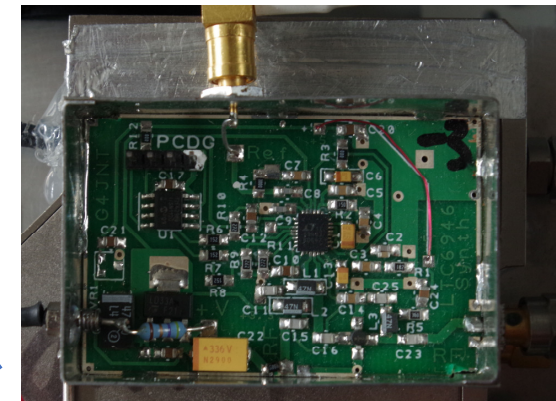
# Low IF With Integer-N synth

- How about a DDS for full frequency agility, upconverted using image reject.
- Band 24 to 24.05 is amateur primary – so image leakage on the low side is unlikely to be an issue
  - It's not as if there are many users down there !
- Keep the numbers simple – 24040MHz LO,
  - LTC6946-3 Integer-N Synth at 6010MHz with 10MHz OCXO (High  $F_{comp}$ )
- 8.xx MHz drive from DDS
  - 20MHz TCXO clock for a 'few Hz' accuracy.
- Image < -25dBc at ~24031MHz



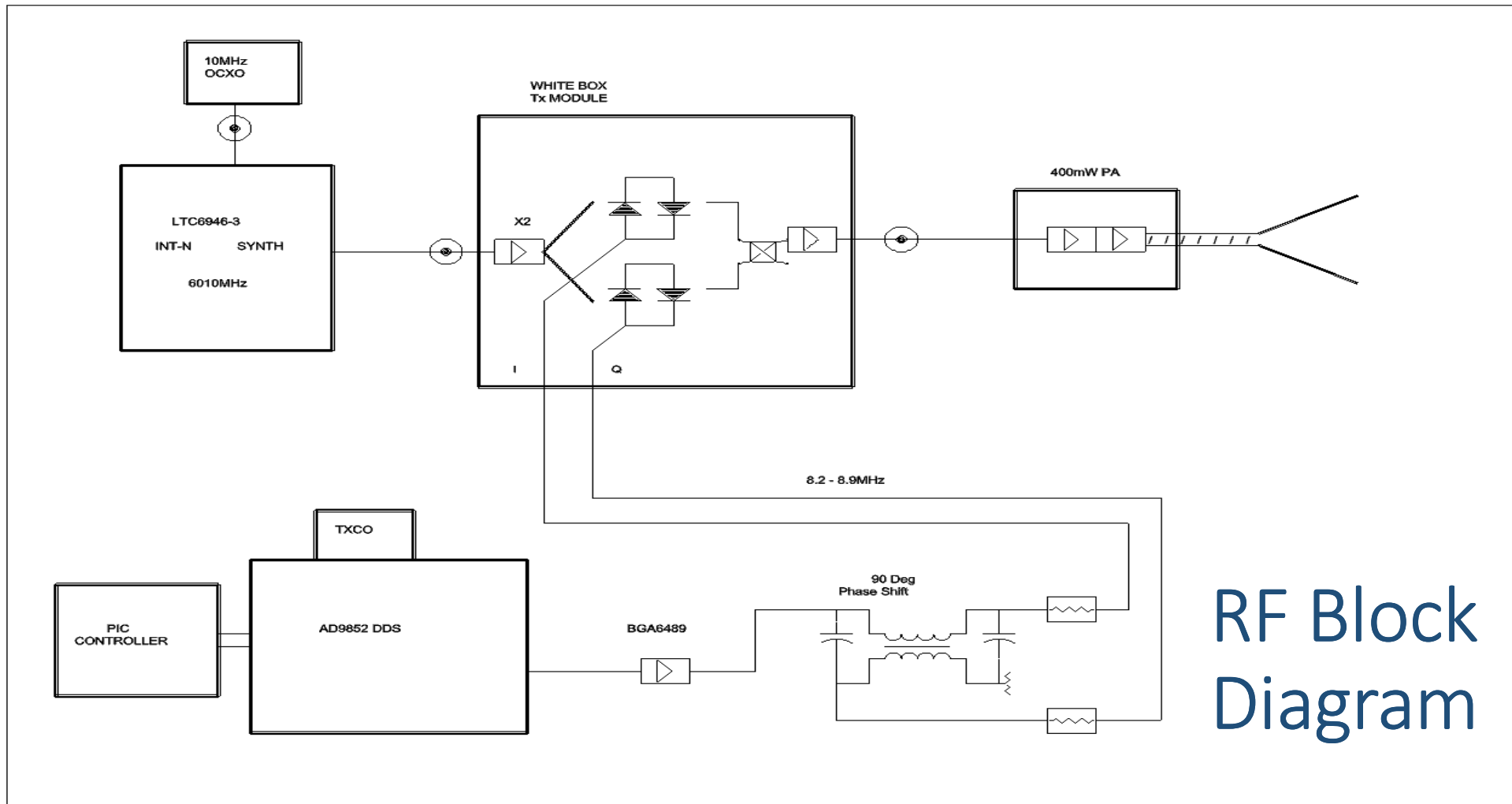


# 90 Degree Hybrid

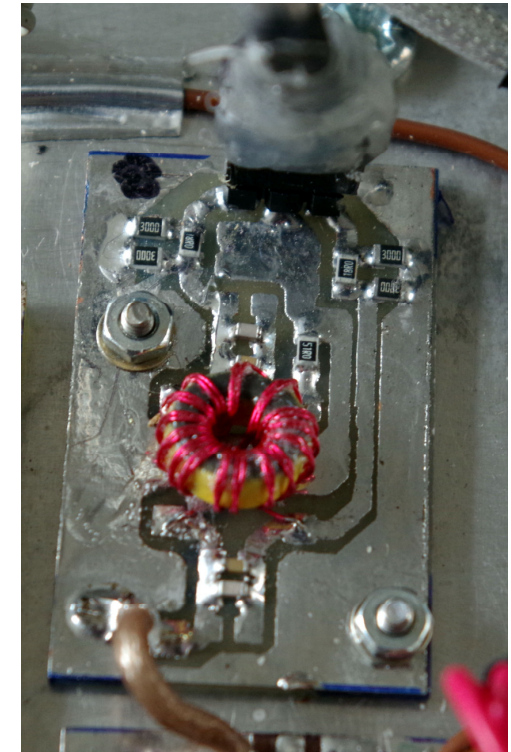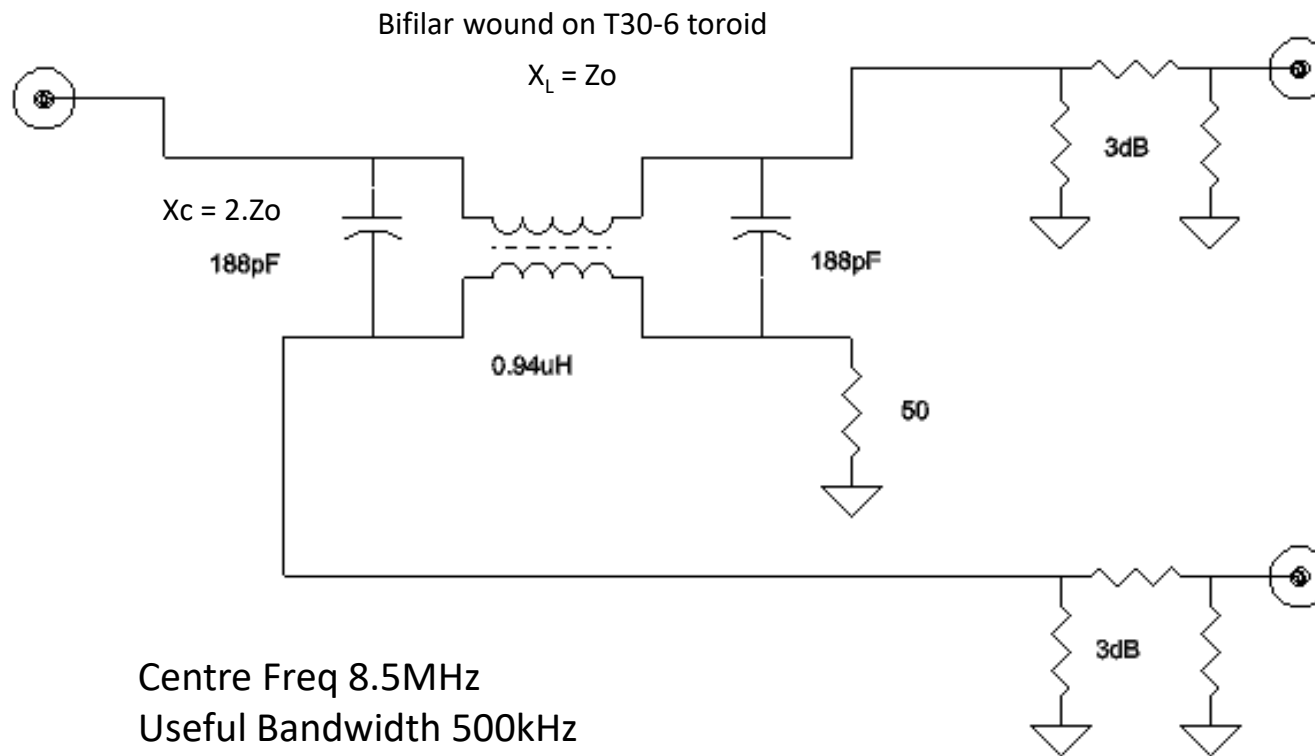



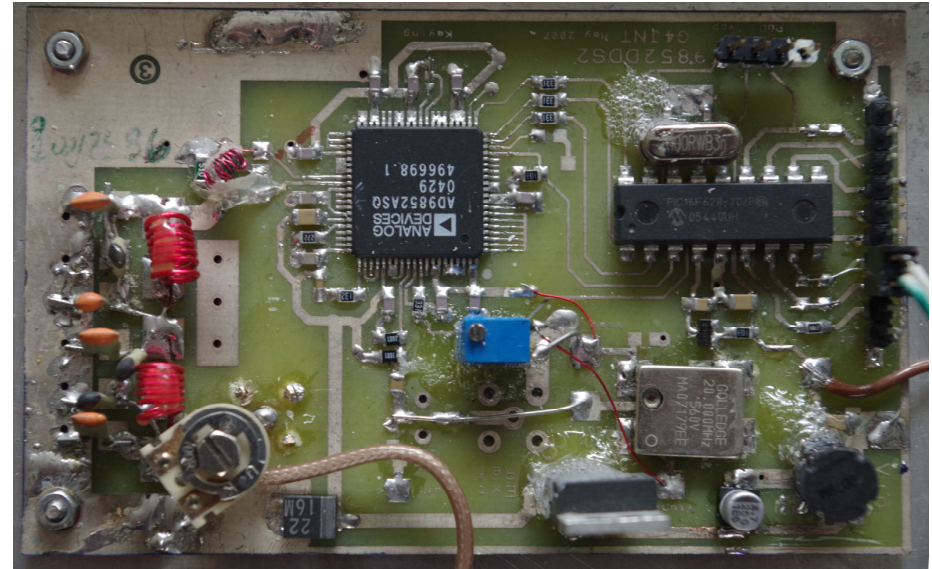
# DDS Source

- AD9852 Module already to hand.
- Plenty of PIC firmware for all data modes
- Offers frequency and amplitude variation
- -4dBm output
- Max drive to diodes is around +12dBm each.



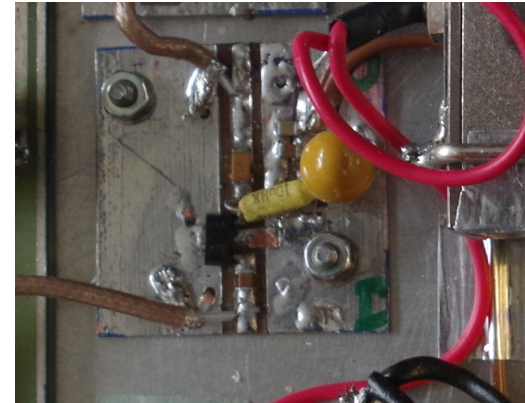
# Gain Block

- Diodes need max +12dBm each
- Quad network has -6dB each channel
- So hybrid needs 18 – 19dBm drive
  
- -4dBm from DDS
- BGA6489 MMIC
- Not intended for this low frequency, but it works!
  - +20dBm  $P_{1dB}$
  - > 23dB gain
- Plenty of gain margin


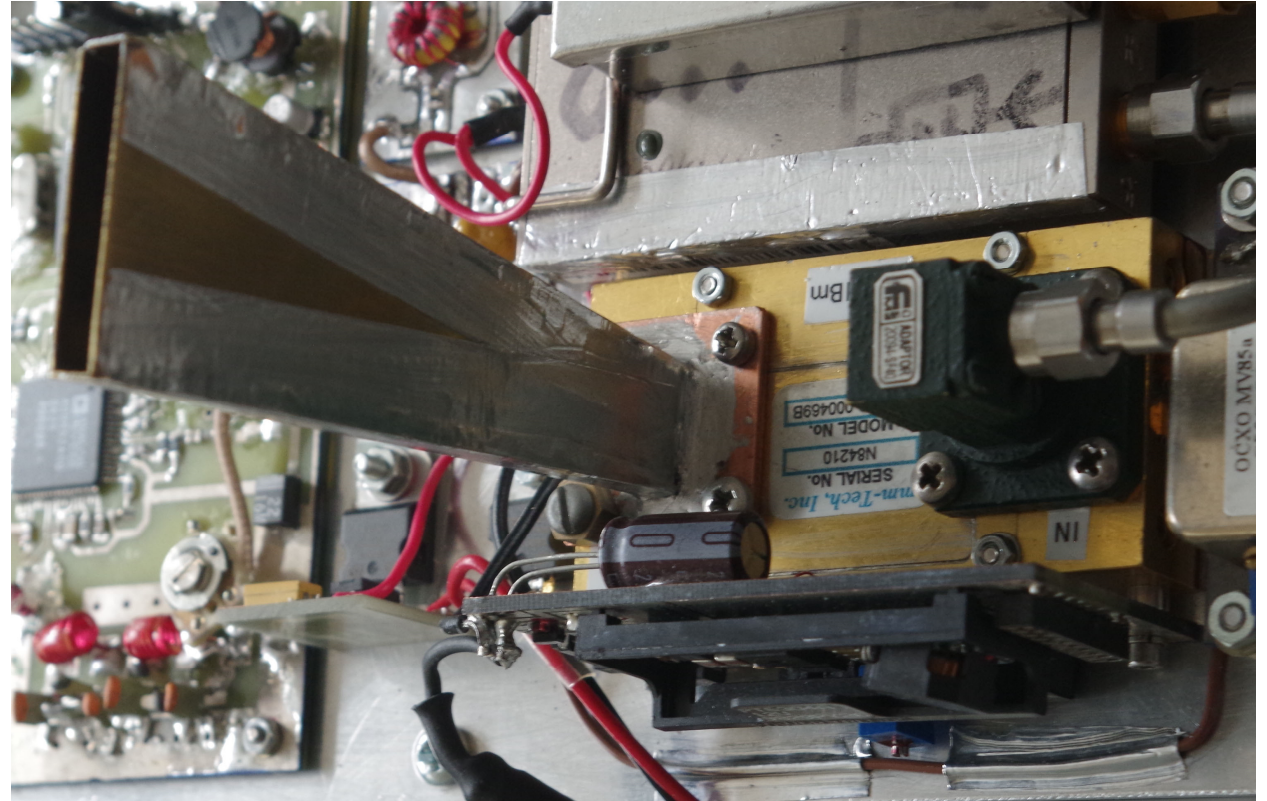
# RF Power Amp

- 400mW (ish) Module from  $\mu$ Wave Roundtable
- Self contained SMPSU with 12V input



# Power Supply

- All modules apart from PA run from nominal 5V
  - 5.2V for WB converter
- First thoughts, 12V to 5.2V buck converter.
- Couldn't get it clean enough, as the 5V goes direct to RF circuitry.
- Two linear converters, LM317 for 5.2V and LM7805 supplied from buck converter to 7.7V
  - Good filtering in dedicated screened box with feed-throughs.
- Total current consumption 1.6A at 13V with OCXO stabilised
- 20 Watts of heat generated

# Cooling



- Traditional solution, metal box with heatsink
  - Waterproofing nightmare
- Plastic box for waterproofing,  $\sim 20\text{W/K}$  across thickness, insignificant
- All modules mounted on thick Al baseplate to share heat dissipation
- Fan inside rapidly circulates air
- All the box surfaces work as heatsink  $0.27\text{m}^2$
- After several hours in summer temperature indoors, surface of plastic box is about 10 - 15 deg above ambient
- Hottest items inside sit at around 45C

# Antenna


- Omni would be nice, but slotted waveguide at 24GHz is not easy.
- H-plane Sectoral Horn is next best compromise
- 9dBi , 20deg vertical beamwidth, wide azimuth
  
- G8AGN Horn design software
  - Latest 'JNT version for Windows
  - Gives cutting templates




# Antenna

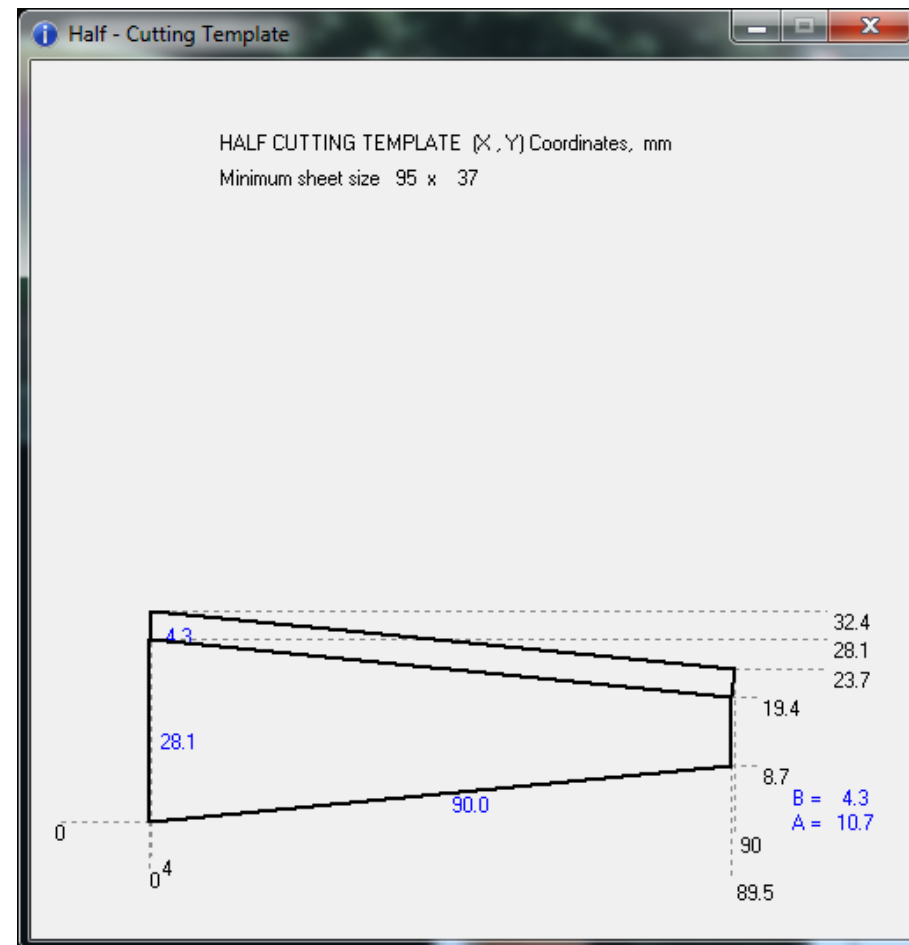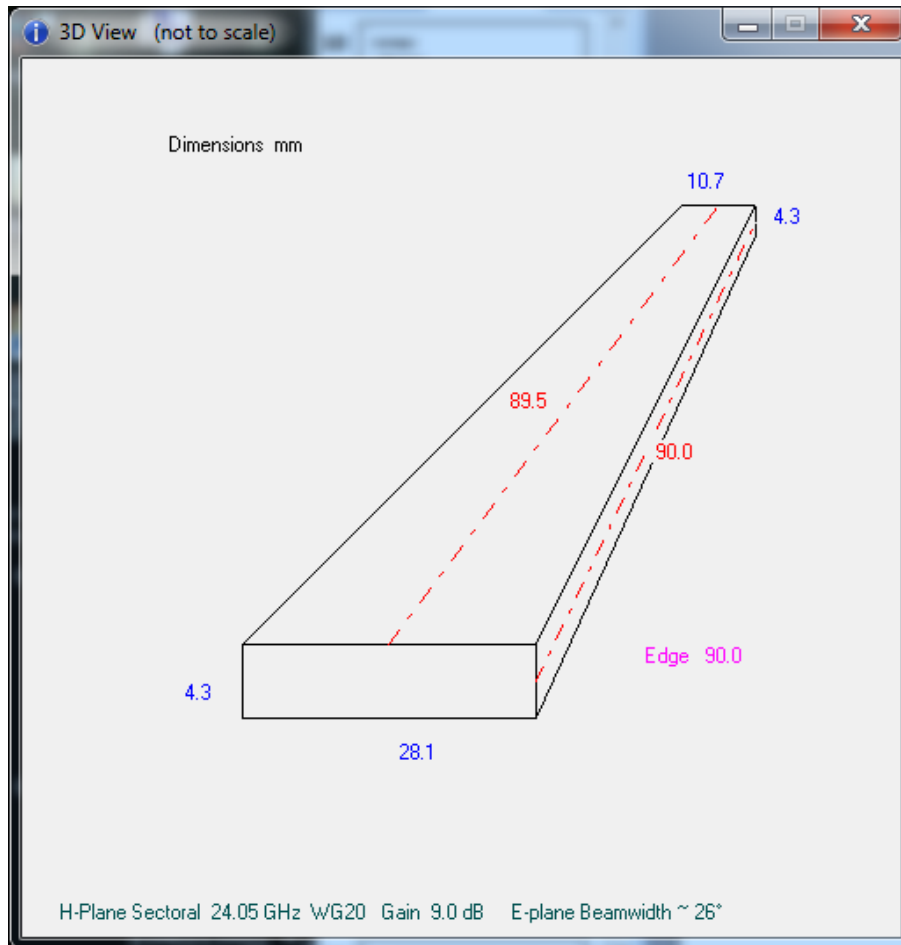
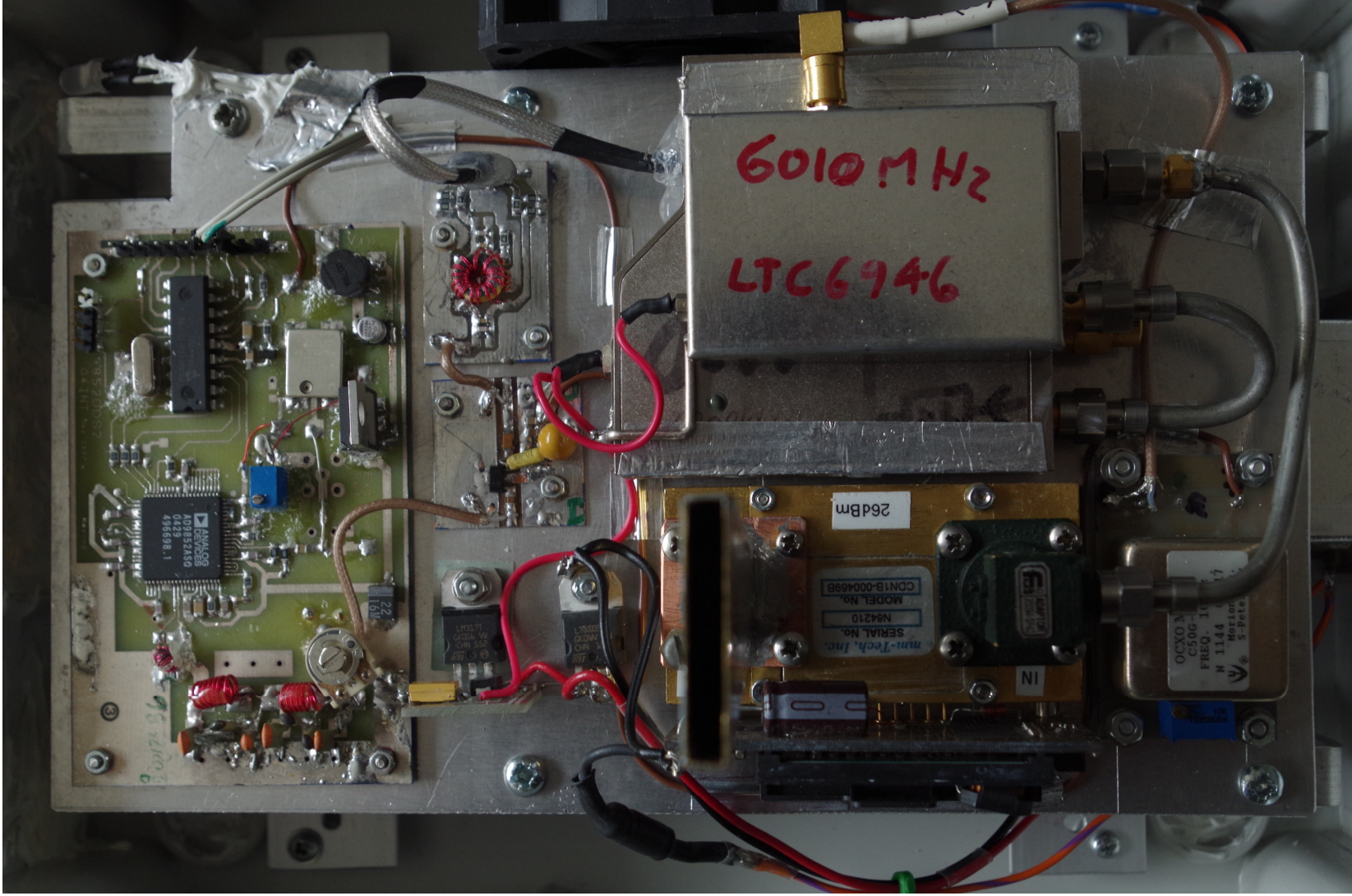
# Modulation

- As this is a sort of ad-hoc setup-and-drive-out beacon with no GPS ...
- For once, and completely contra to normal 'JNT-think ...
- An audio modulation rather than digital mode is called-for
- And just plain CW will never be an option
  
- Reprogramme the DDS with 3Hz increment every 0.8ms generates a sweep. Reset after 700 steps gives 2100Hz chirp every 0.56s
- And... might as well ... a CW ident, using raised-cosine ramp. 
  - Spot the phase noise and AGC pumping



6010 MHz  
LTC6946

26dBm

mm-Tech, Inc.  
SERIAL No. N94210  
MODEL No. CDN1B-000465B

OCXO N  
C506-  
FREQ. 30  
N 1144  
Horizon  
S-Pete


AD9852ASD  
0428  
496698.1

6010 MHz
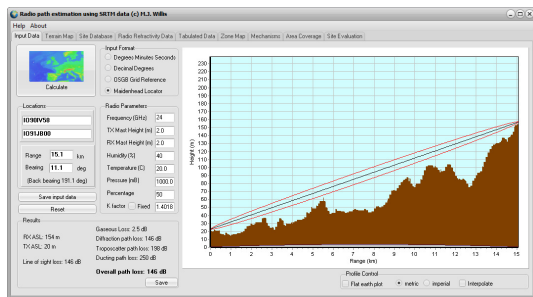
# Results

- At 24028.5 MHz Opposite sideband leakage, -25dBc
- At 24048.8 MHz best value -32dBc
- No trimming of I/Q paths; no doubt that could be improved
- Some close-in DDS spuri around -60dBc
  - Changes rapidly with the sweep
- No other spuri from synth
- Mounted on my mast, I can receive it at Cheesefoot Head 5/9





# Cheesefoot Head

A view from behind.

02:00  
12 Aug 2017

