

MODERN FREQUENCY SYNTHESIZERS

Andy Talbot G4JNT

RSGB Convention 2014

A Synthesizer is a very powerful
machine,


It can generate all frequencies once,

And most of them twice,

Simultaneously.

(G3RZP, sometime in the 1980's)

The Basic Integer- N Synth

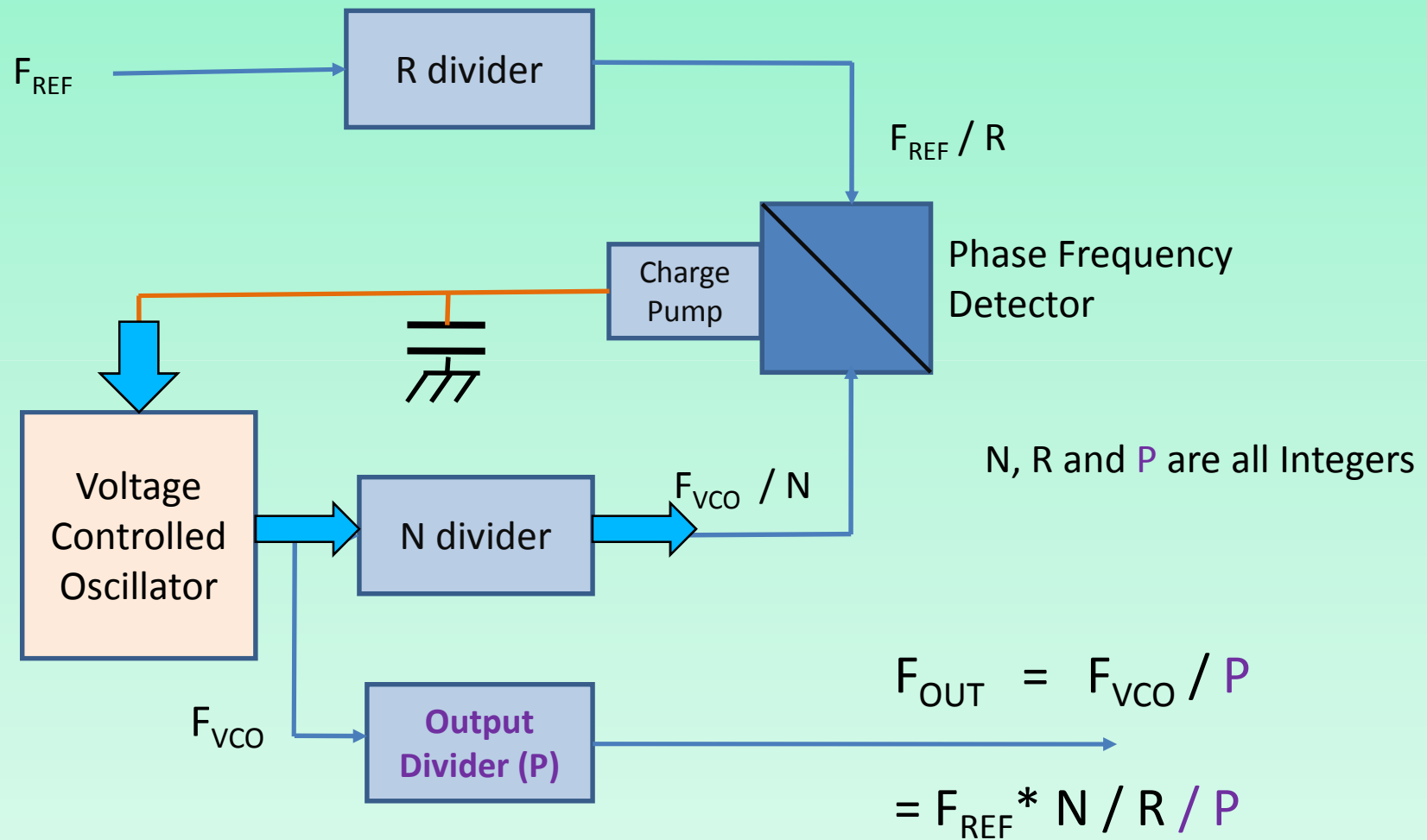

- Tuning Grid in steps of F_{COMP} / P
- Loop time constant / bandwidth, spuri all depend on F_{COMP} which is defined by the Step Size
- Useful for
 - Fixed sources eg. transverter LOs
 - Channelised operation
 - Multiplier from a variable input , eg. DDS, VFO
- $F_{\text{OUT}} = F_{\text{IN}} * N / R / P$: Non-integer Freq multiplier


Phase Noise

- The Performance Limiter
- Generated as the loop continually adjusts itself
 - Several Sources
- Noise appears as FM / phase jitter on the carrier.
 - INSIDE the Loop Bandwidth it is determined by the REFERENCE alone
 - OUTSIDE the Loop Bandwidth it is determined mainly by the VCO and its drive circuitry.


Loop Bandwidth

- The Loop Filter defines the loop performance
 - Ideally set at the point where Reference and VCO noise cross over BUT
 - Has to attenuate comparison frequency sidebands
 - Prevent External influences (microphony)
 - Determines Lockup Speed – several cycles
- Often want as high a loop BW as possible,
 - Subject to loop components themselves not contributing.
 - Filter Order, good design techniques allow 4th order filters
- Programmable Charge Pump allows post design tweaking

The Basic Integer- N Synth

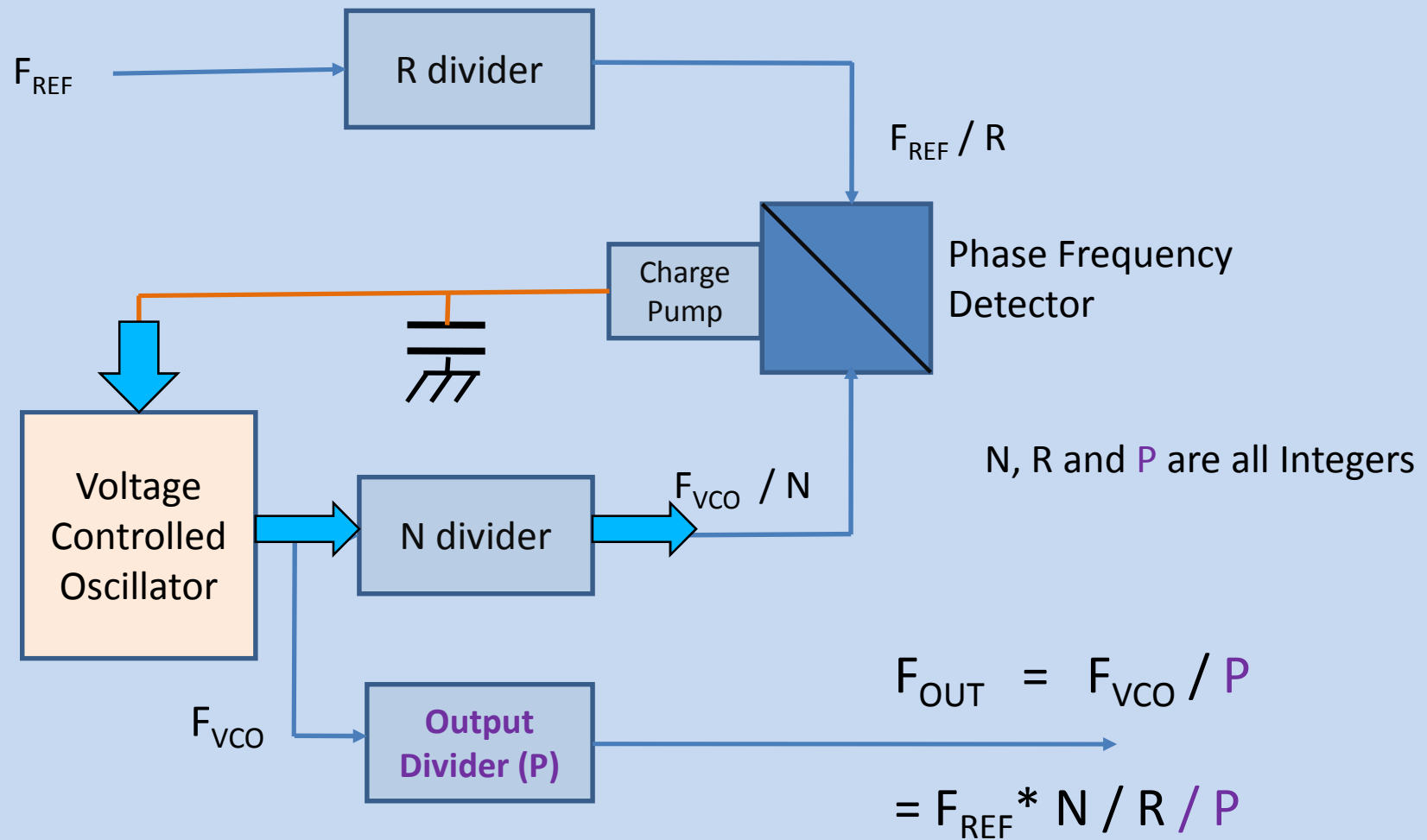

Loop Filter (third order)

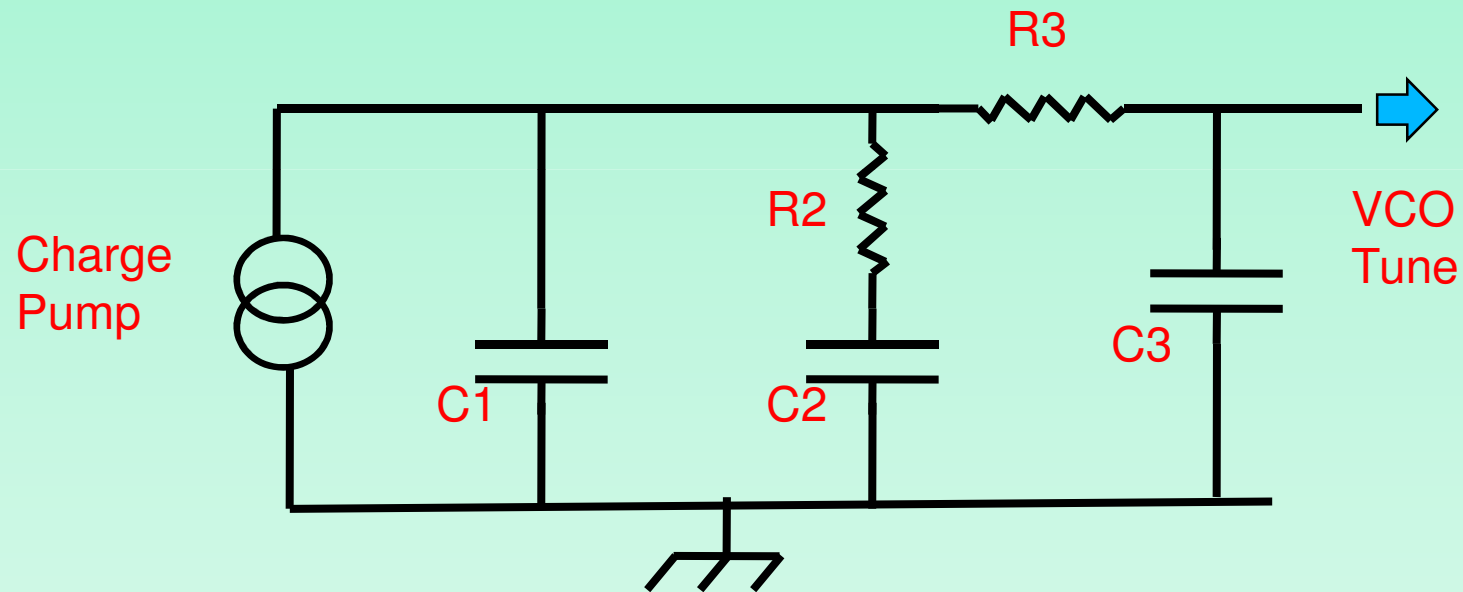


Phase Noise continued

- Far-out phase noise is mostly a strong / adjacent signal problem. You need to decide how important that is:
 - On Transmit: spuri, cause QRM, regulatory
 - On Receive: Strong signals, reciprocal mixing
- Close in, Phase Noise affects audibility, sounds like rumble.
 - Use a low jitter good quality reference
 - Rarely a problem with latest generation synth chips
- Output Divider reduces Phase Noise by N^2
 - So a GHz synthesizer divided down can give a good HF or VHF source

dBc/Hz

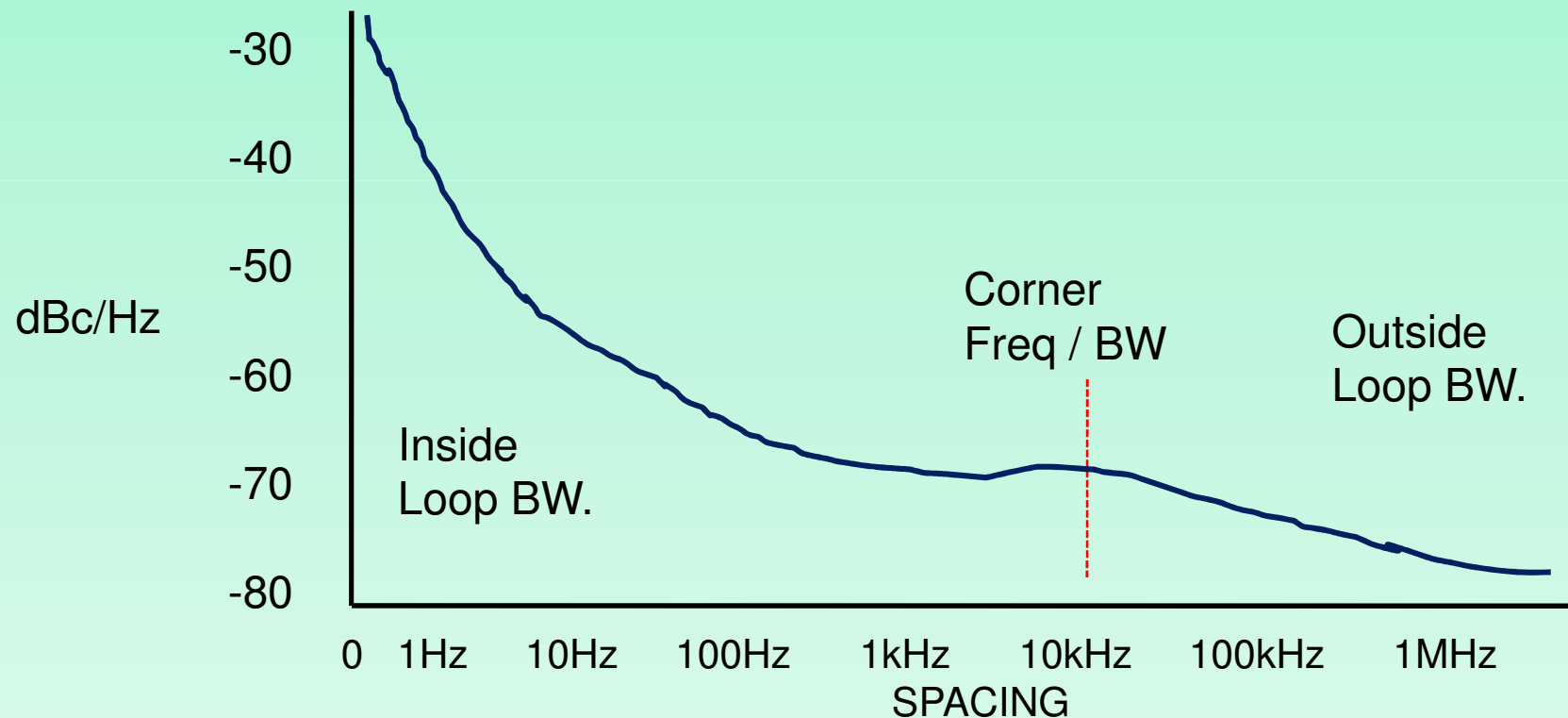Relative amplitude of the phase noise, in a 1Hz bandwidth referenced to the carrier. Specified at a particular spacing, in Hz, from that carrier



Latest Advances in Modern Devices

- Phase Frequency detectors work to many MHz
 - High F_{COMP} means high loop bandwidth
 - Improves close in phase noise
 - Programmable charge pump
- Integrated output divider
 - Gives UHF to low VHF coverage and smaller steps
- Integrated VCO on the chip
 - (GHz only, but *can* be octave coverage)

Internal VCO

- One chip Synthesizer
 - No Need for separate VCO hardware / module
 - Packaged VCOs often more expensive than the synth chip itself
 - No High tuning voltages
 - Many packaged VCOs need 20V
- BUT
 - Higher far-out Phase Noise due to lower Q silicon resonator (outside loop bandwidth)
 - Need more programming / setting up


Internal VCO

- Wide(ish) tuning range,
 - Needs several chip variants
 - Removes Tuning voltage limitation
- Auto calibration pretunes the VCO
 - Typical sensitivity 20 – 40MHz/V in spite of 100's of MHz tuning range
 - The chip has to be “told” the value of F_{REF}
 - Auto Recal whether you like it or not = glitches when frequency is changed (sometimes)

A Few useful Integer-N chips

- LMX 23xx, 24xx (many family members)
 - Obsolete, but the workhorse of much surplus stuff
 - 100MHz to 2.8GHz
 - F_{COMP} to 1MHz
- ADF4110/3 is pin compatible with LMX2326, and goes to 4GHz
- LTC6946 Internal VCO,
 - 3 overlapping band variants 2.2 – 5.8GHz
 - Output divider, 1 – 6, so goes down to 370MHz
 - F_{COMP} to 100MHz
- *There are lots of others out there.*

Avoid Sat-TV Type Chips such as SP6289

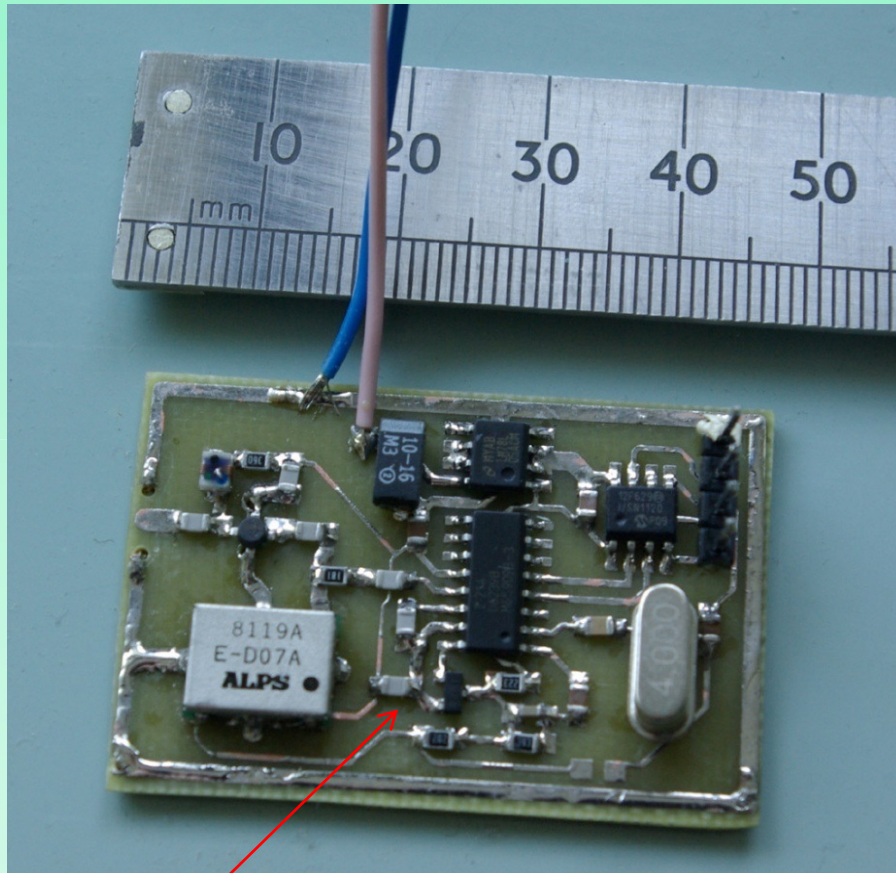

External NPN Charge Pump Amplifier
allows high tuning voltage (30V)

Low F_{COMP} - fixed prescaler

Typical 8kHz

Low Loop Bandwidth (100Hz)


Large Step size (125kHz)

Poor Phase Noise

**Totally and utterly useless for
narrowband designs**


Worth using if you can find them

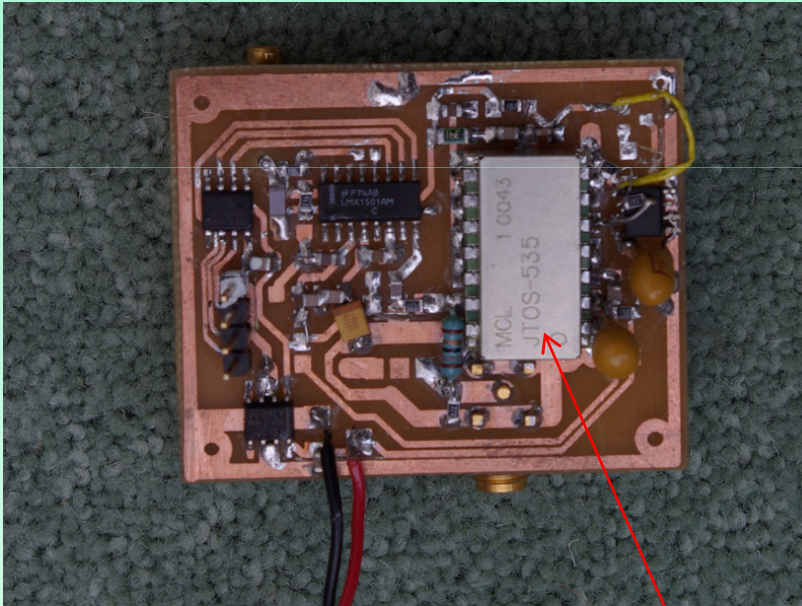LMX1501 Very Obsolete,
but OK for V/UHF.
Simple programming




Packaged
VCOs

LMX2326

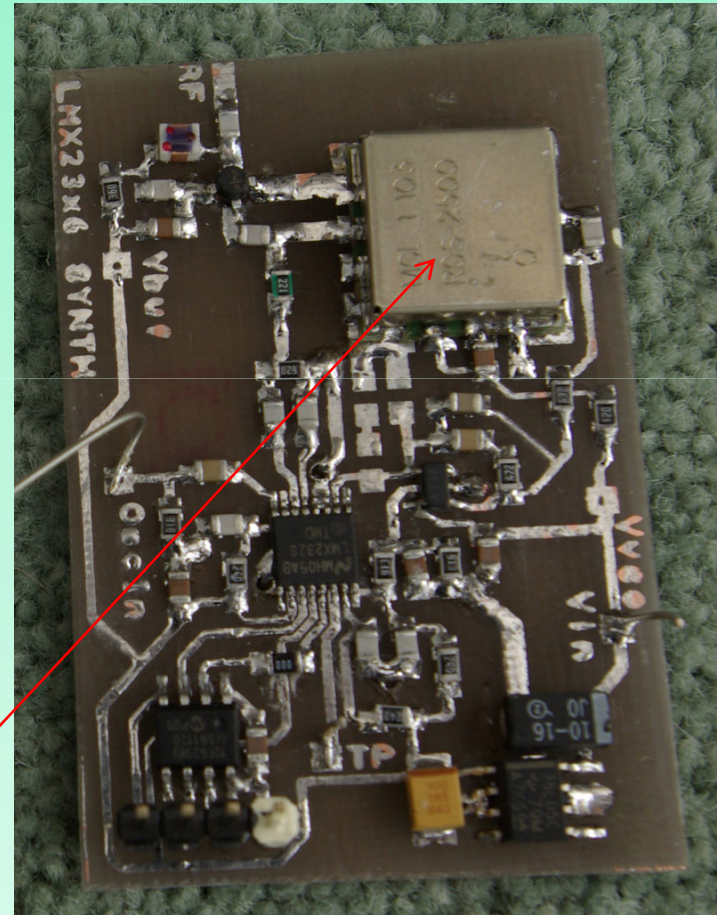


There are many others

LTC6946, integrated 3-6GHz VCO

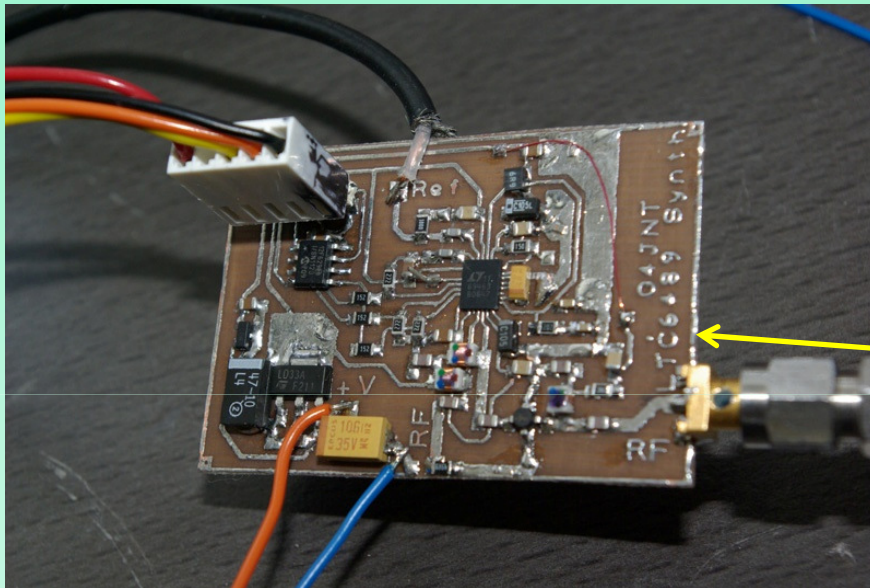

Spot the typo !

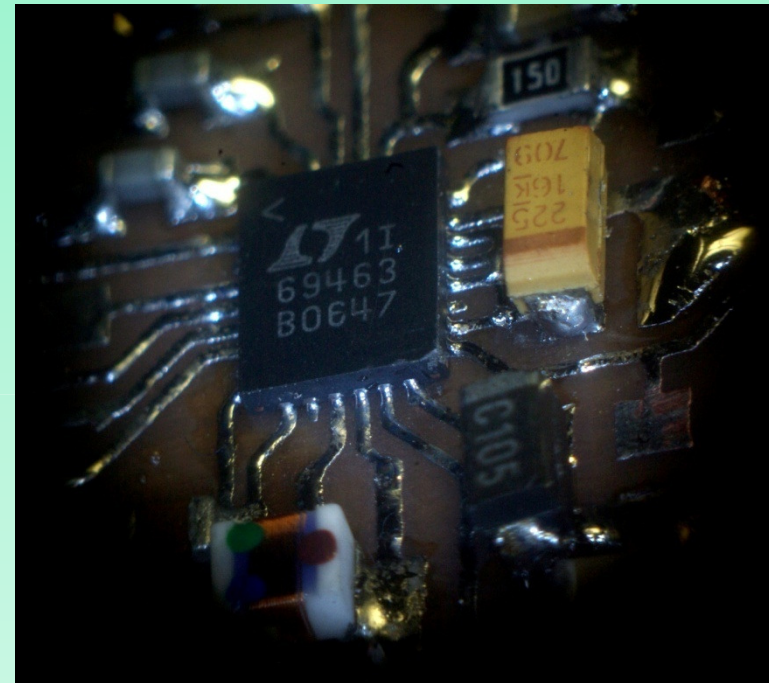

28 pin LQFP package
Home built PCB, chip installed using
the solder-wipe technique with liquid
flux

Used by GW4DGU in 10GHz Transverter LO

BUT


Integer-N designs still
only offer a coarse
frequency setting grid.

$$F_{\text{COMP}} / P$$

The Next stage - Tiny steps

- A low F_{COMP} is not feasible if we want to keep loop bandwidth as high as possible
 - 10Hz steps would need 1Hz bandwidth – 20s lockup!
- Generate high frequencies and divide down - limited use
 - Although for LF, dividing by 1000 - 10000 works.
- Divide down and mix,
 - Complicated, spuri, hardware filtering
 - Yesteryear's solution
 - Many Commercial & amateur radios used triple loop synthesizers for 10 or 1Hz steps.
- DDS + PLL multiplier: Works, but spuri can be bad.
- So Use ideas learned from DSP, Fast processing, filter out the crud!

The Fractional-N Synth

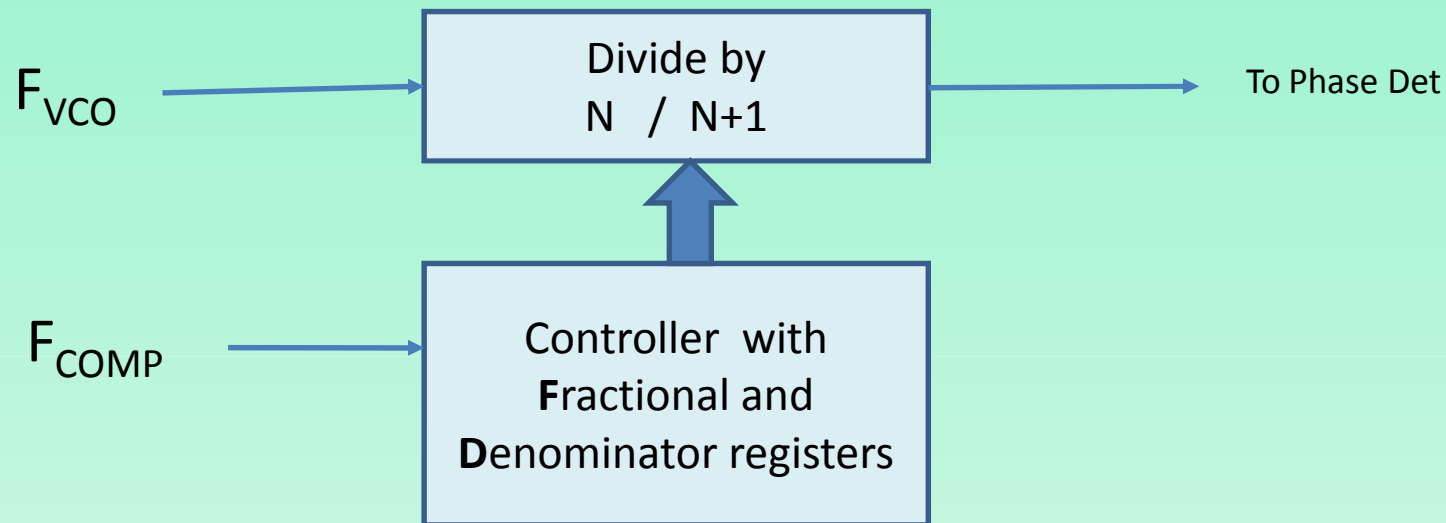

Periodically change the value of N to $N+1$, F times out of every D ,

$$N' = N + F / D \quad F_{\text{OUT}} = F_{\text{COMP}} * (N + F / D)$$

Fractional counter runs at F_{COMP} which can be many MHz

Tuning grid = F_{COMP} / D . Large D = small tuning steps

BUT !

With this simple route
There will be multiple SPURII at the grid
spacing.

They can be controlled.
Their amplitude can be made low *enough*.
They can be made to just look like phase noise.
Usually
On a good day

‘Real’ Fractional-N Synthesizers

- Use $N / N+1 / N+2 / N+3$ Called “ **Sigma-Delta** ”
 - Shift between them in a pseudo random way
 - Dither to spread out the spuri.
 - Do clever stuff
- All this happens inside the chip
- As well as other things the manufacturers don’t want to tell us!
- They let the users programme everything, optimising by trial and error. *Is this a cop-out?*

The Result

- A 22 Bit Denominator (4194304) gives fine steps even with $R = 1$, where $F_{\text{COMP}} = \text{Input Reference}$
 - 10MHz in
 - means step size can be 2.4Hz
 - We can define specific step sizes for Multi-Frequency data modes. Eg 5.3833Hz for JT65B ($D = 1857596$)
- High F_{COMP} means Fract-N jitter is kept low
- Loop bandwidth stays high. 20 – 100kHz typ.
- THE IDEAL SOLUTION TO EVERYTHING ?
 - Almost ----- but not quite!

Limitations

- Problems around low and max values of F ,
 - I.e. Close to integer values
- Also some low small integer ratios, like 0.6666666,
- Manufacturers provide a host of user settable options.
 - Usually possible to find one that works
 - **Unless you can't**

Just a few of the Synth Chips around

Integer-N

Type No	VCO	Freq range	O/P Divider	Vcc [max] (Vph)	Availability
LMX2326	External	100 – 2800	-	5 (5)	Obsolete, found on Surplus PCBs
ADF4110 / 3	External	80 – 550 / 4000	-	5 (5)	RS £4.50 Pinout = LMX2326
ADF4118	External	100 – 3000	-	5 (5)	RS £3.20 Pinout = LMX2326
LTC6946	Internal (3)	2240 – 5790	1 – 6	3.3 & 5 dual	£12 ++ US Stock Farnell

Fractional-N

Type No	VCO	RF I/P Freq	Fract Res bits	O/P Divider	Vcc (Vph)	Availability
LMX2470	External	500 – 2600	22	-	2.5	RS £4.30
LMX2487	External	3000 – 7500	22	-	2.5 – 3.3	RS £5.30
LMX2541	Internal (6)	1990 – 4000	22	1 – 63	3.3 (3.3)	Digikey / Mouser ~\$10
ADF4150	External	500 – 5000	12	1,2,4,8,16	3.3 (5)	Farnell £5.40
ADF4150HV	External	500 – 3000	12	1,2,4,8,16	3.3 (30)	Farnell £6.20
ADF4156	External	500 – 6200	12	-	3.0 (5)	RS / Farnell £5.30
ADF4159	External	500 – 13000	25	-	1.8 & 3.0 (3)	
ADF4351	Internal	2200 – 4400 (full octave)	12	2^N to 64	3.3 (3.3)	Digikey ~\$10
LMX2492	External	500 - 14000	24	-	3.3 (5)	Manuf, (Free samples)

A Few Spectral plots.


Downconverted using overtone crystal oscillator LOs
and SDR-IQ.


Good quality 10MHz TCXO is the reference
– unknown phase noise

FractN Spurii at 432MHz

Third and Fourth order Sigma-Delta


Note...
20dB/div.
Sidebands -70dBc

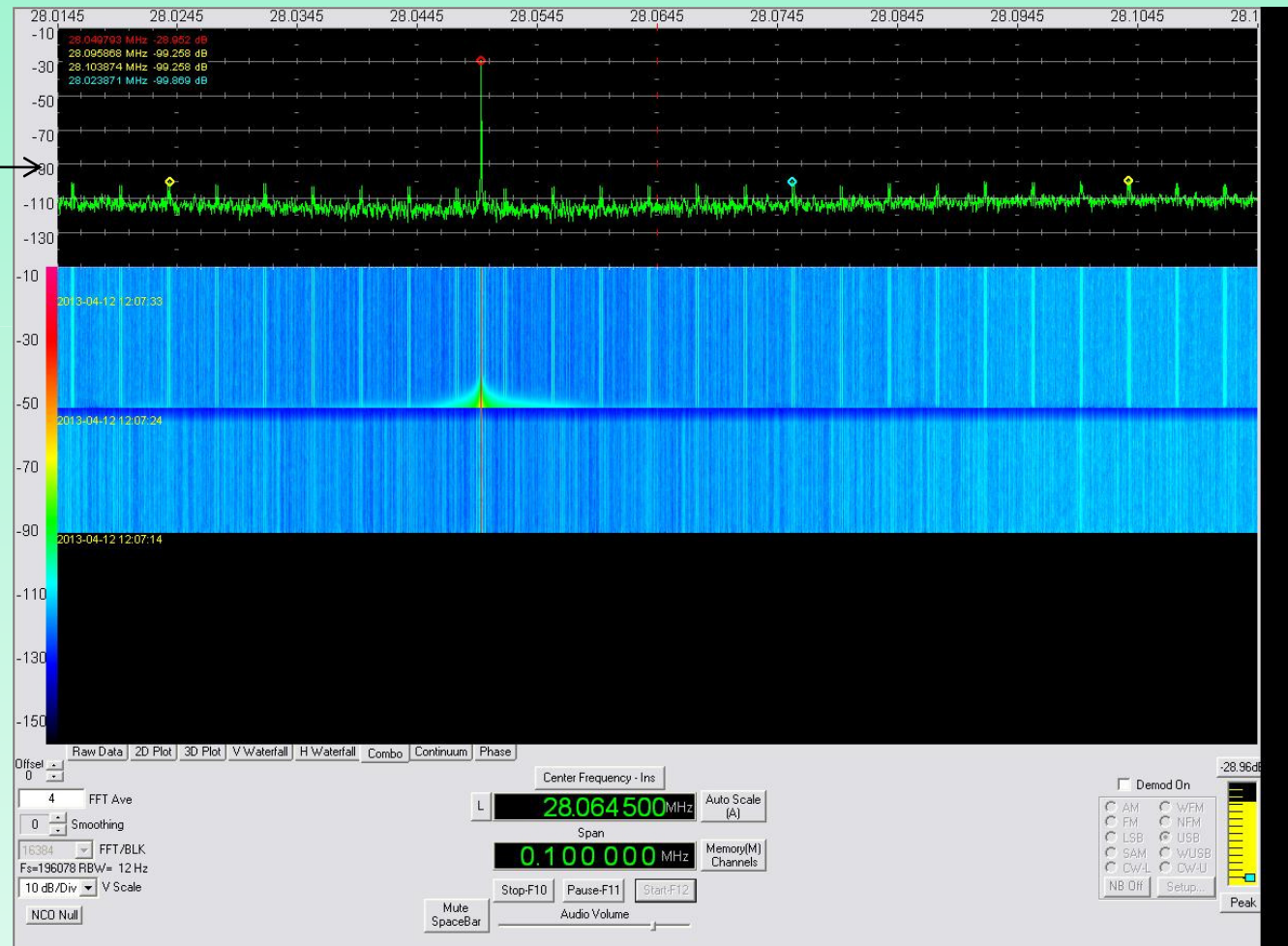

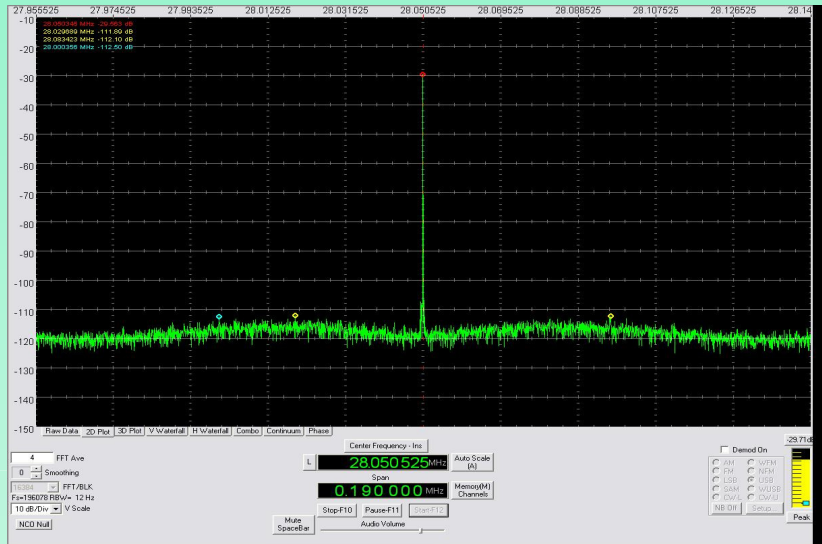


432MHz
(2.6GHz /6 OP Divider)

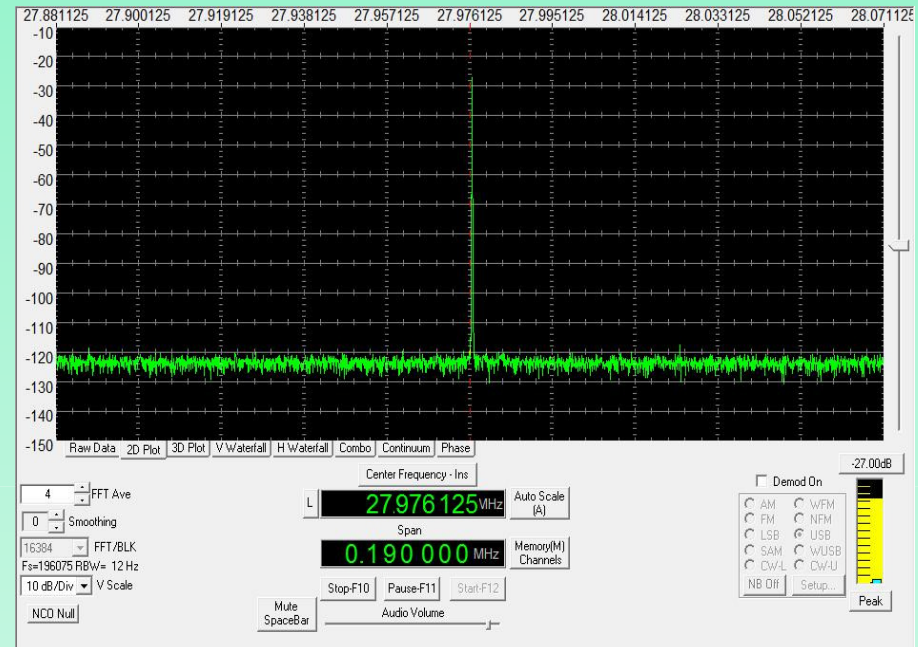Both plots noise B/W = 12Hz.
dBc/Hz is 11dB Lower




Compare with 432MHz
from a crystal source

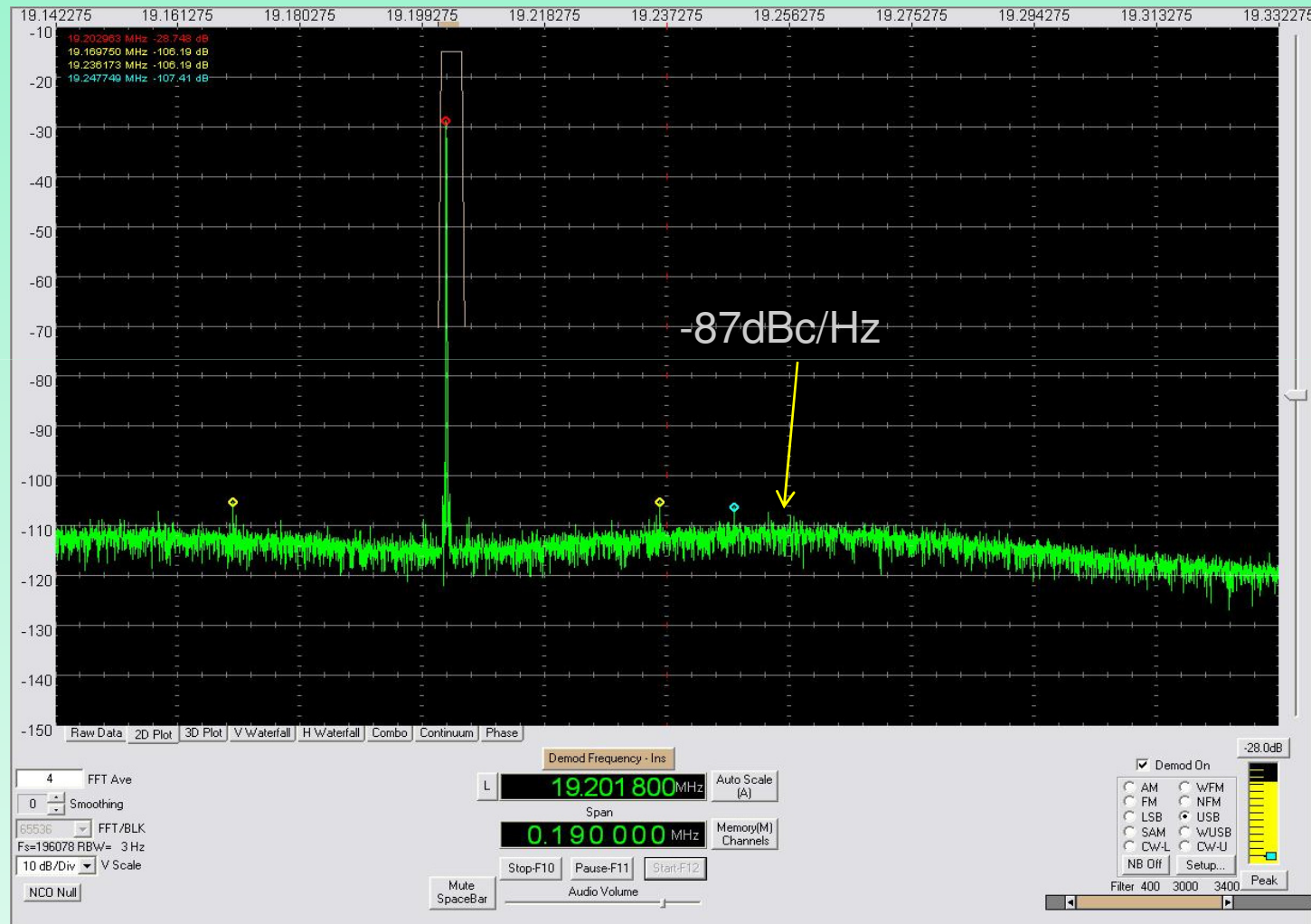1296.2MHz (5Hz step resolution) (Wide 80kHz loop bandwidth)




5760MHz (LMX2541, 2.88GHz + Doubler)


Loop filter 30kHz BW

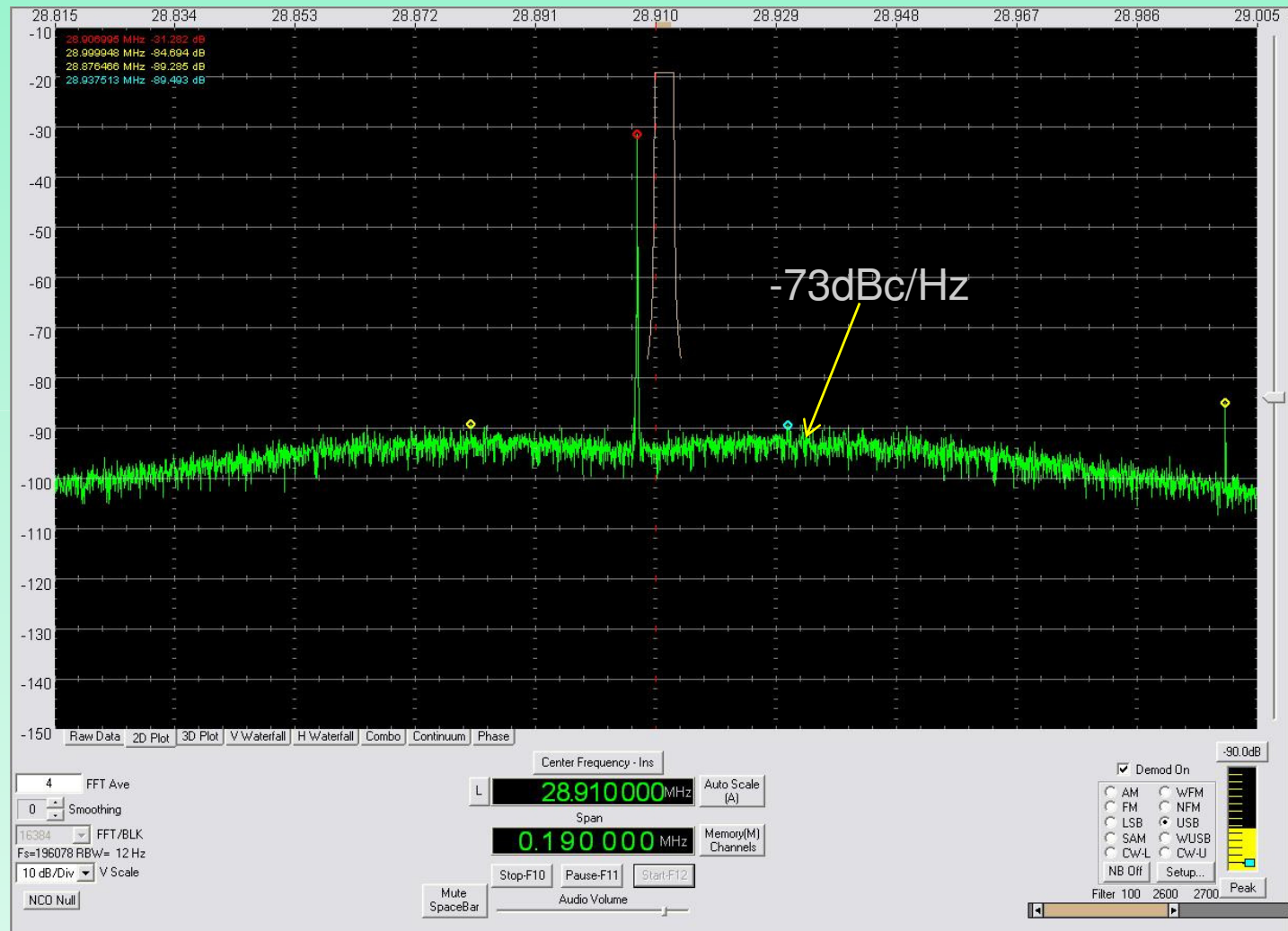

144MHz Close in (1.5Hz noise B/W)

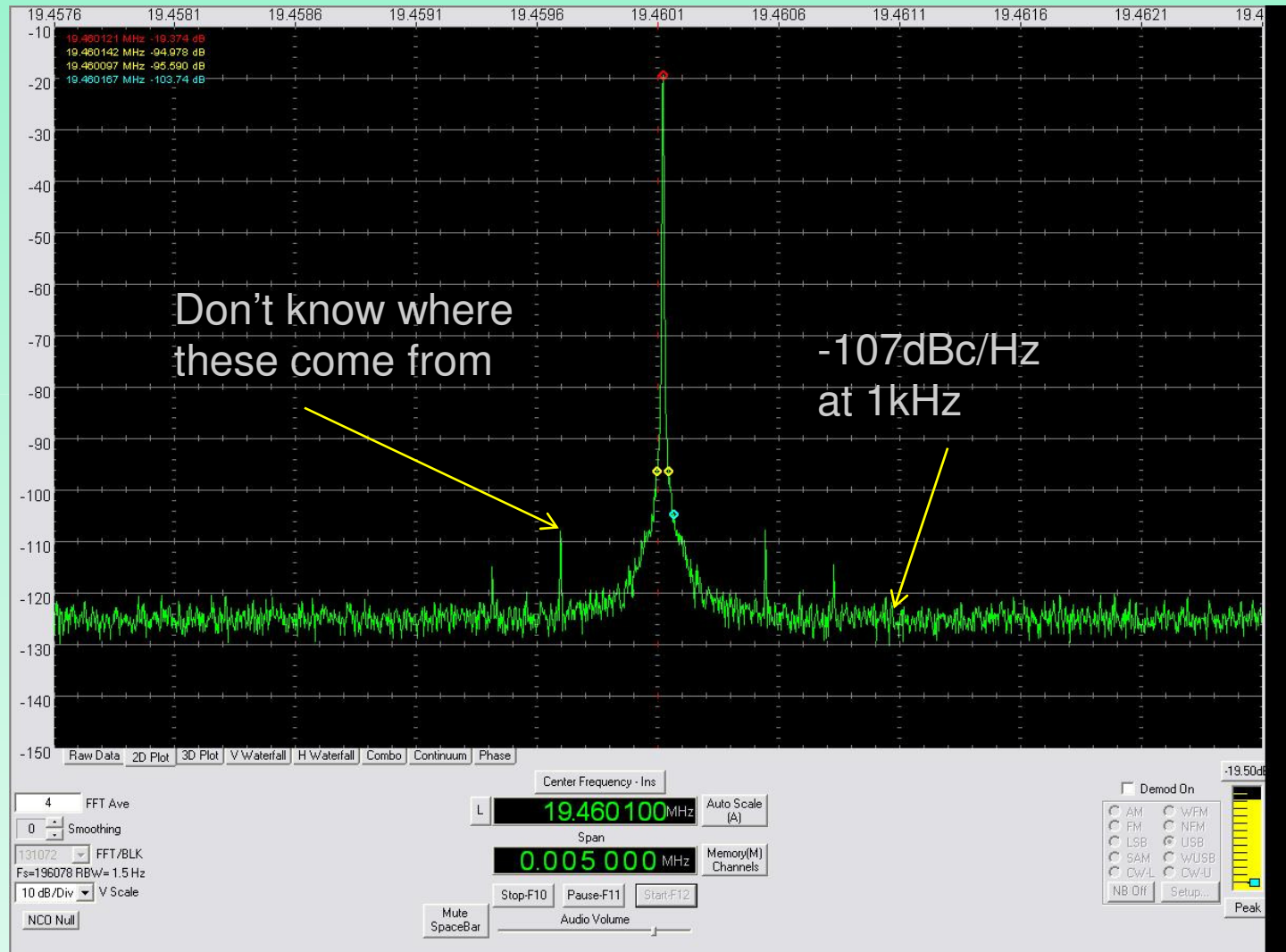

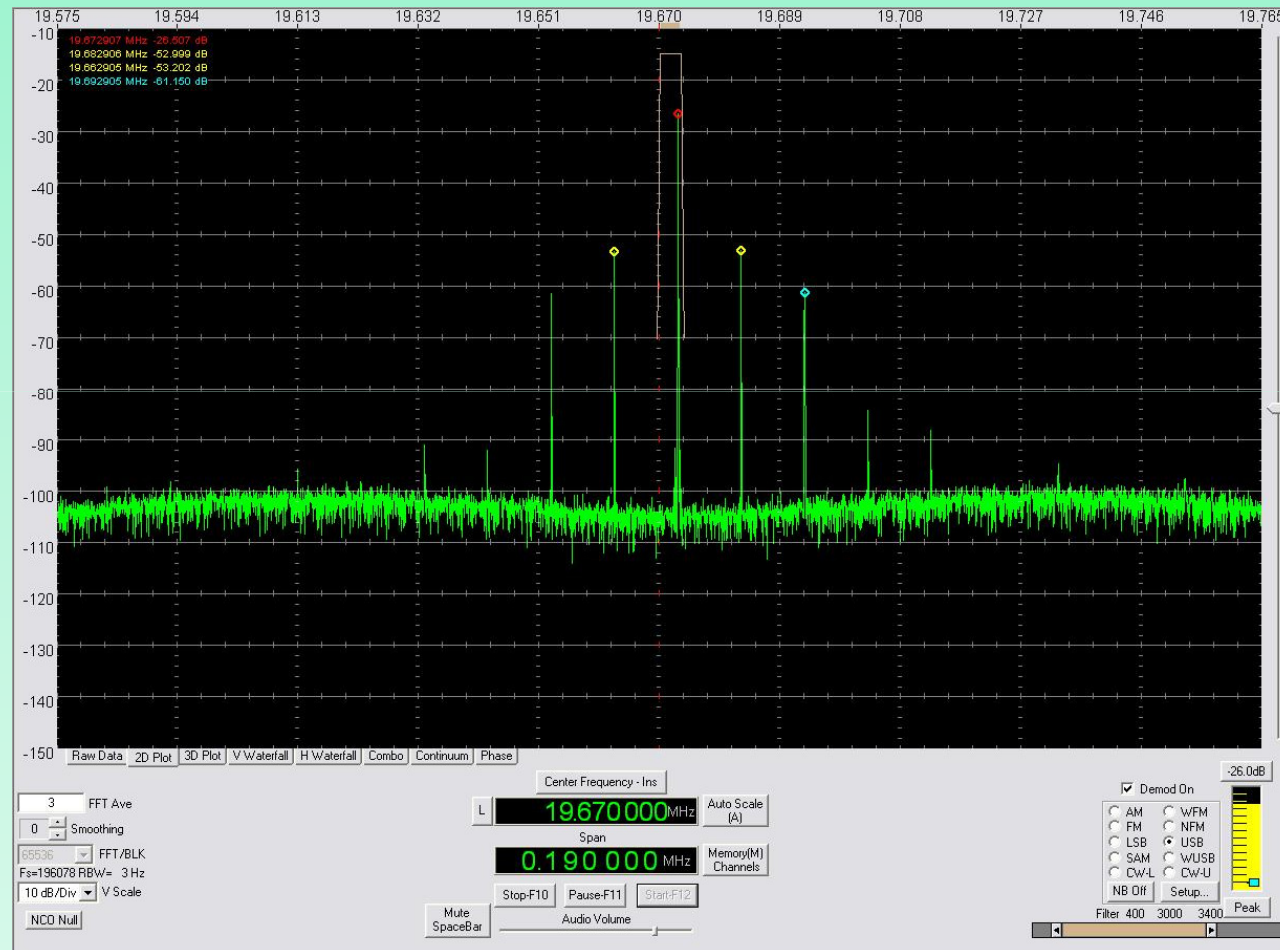Found by accident , an unfortunate choice of F/D ratio.
1296.67MHz 80kHz loop bandwidth



A convenient point to end if time is short.

If not...

A Few Practical Designs


Practical Designs

- External VCO
 - LMX2470 up to 2.5GHz
 - LMX2487 up to 6GHz (both 22 bit D)
- ADF4150, 5GHz
 - 12 Bit Denominator (medium size steps)
 - Output divider /2 , /4 , /8 , /16
- Lower VCO limit for all these is 500MHz


Tuning Voltage Limits

- Charge Pump V_{dd} (or a rail not much higher)
 - 3 to 5V is typical
 - Except the ADF4150HV 30V Why did they use the same type number ?
- External OPAMP / active filter
- LM6211 is designed for the job
 - 5 pin
 - 20MHz bandwidth
 - Rail to Rail


Loop Filter

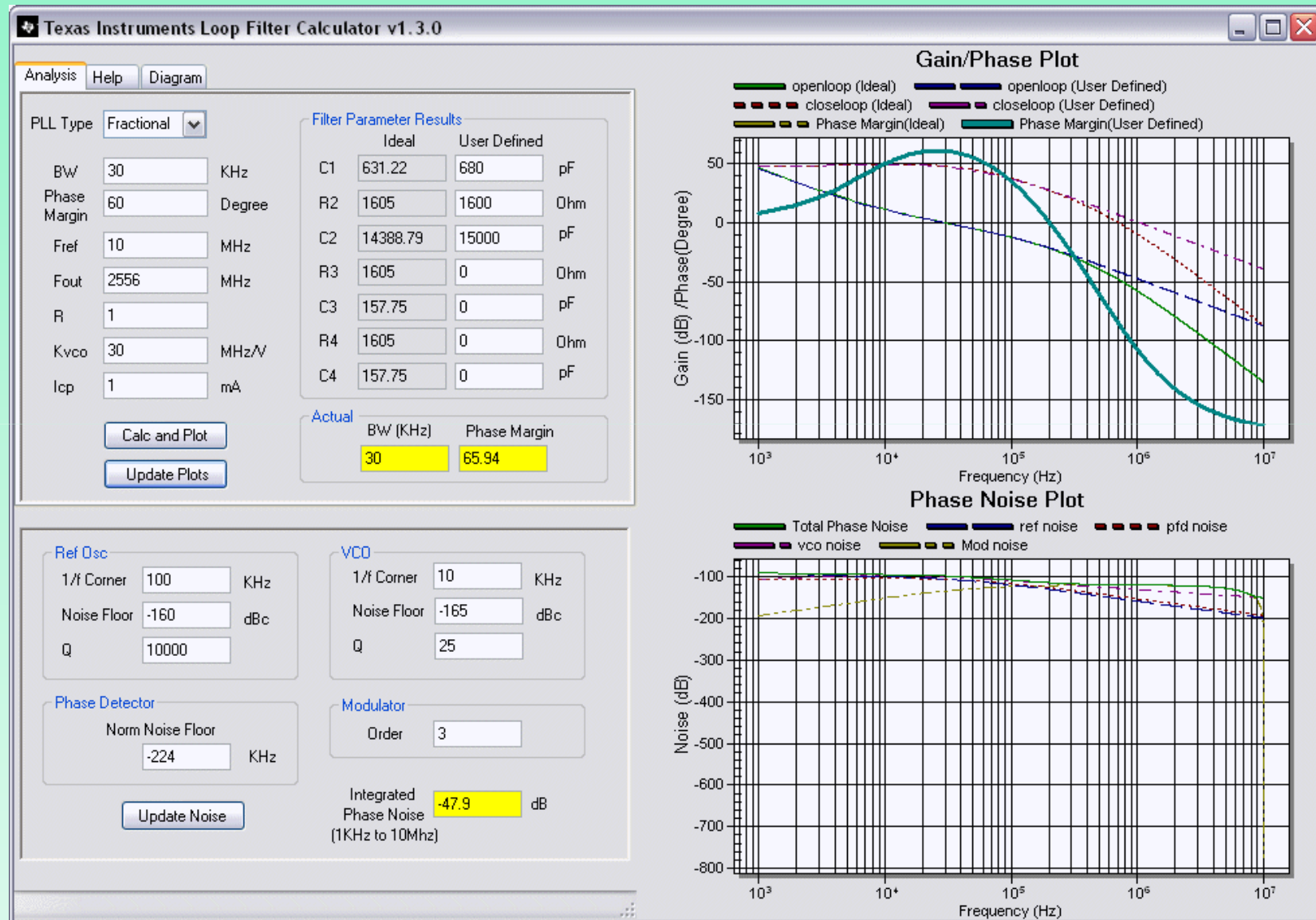

Practical Hardware - LMX2470

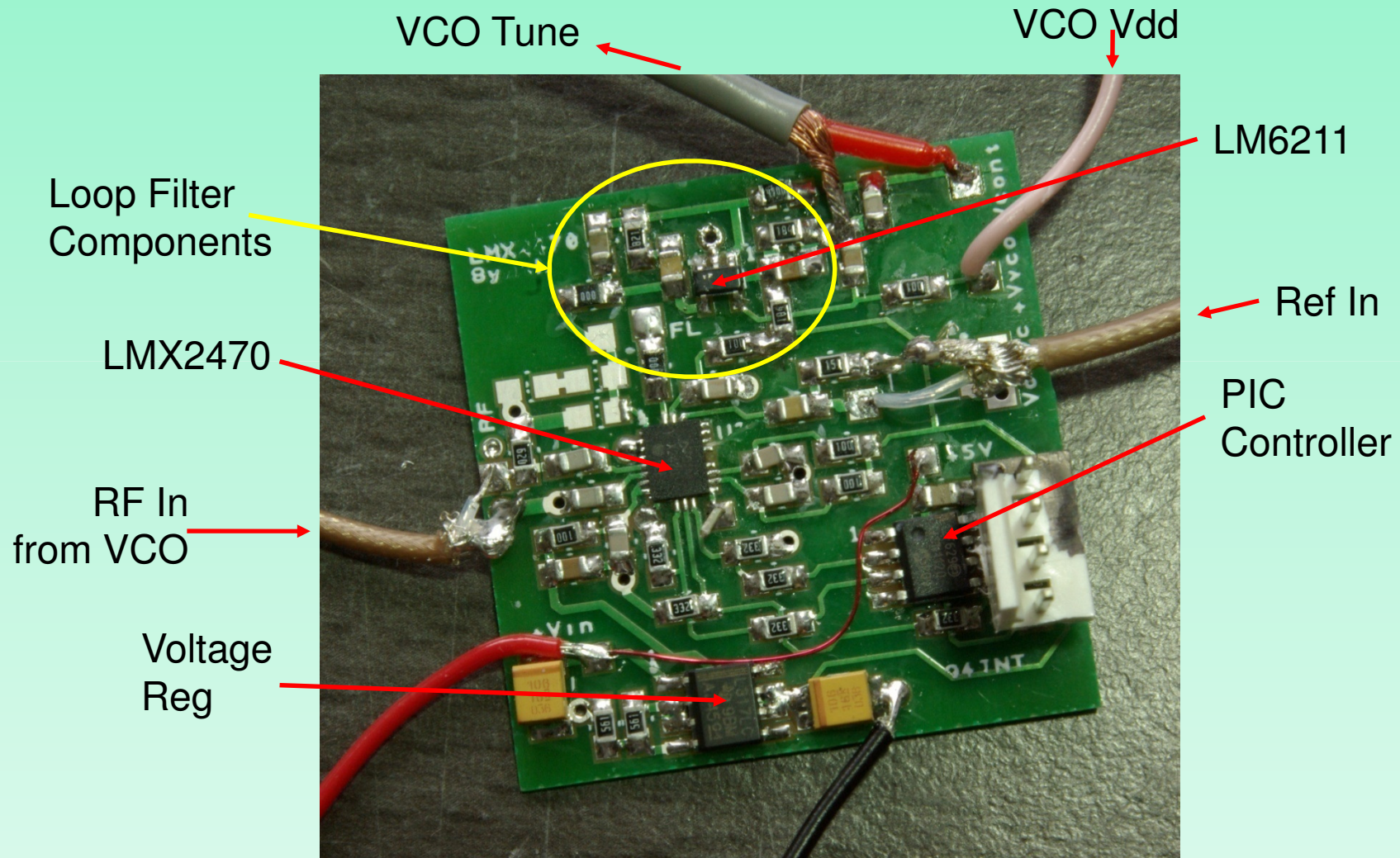


It's easy with an Internal VCO!

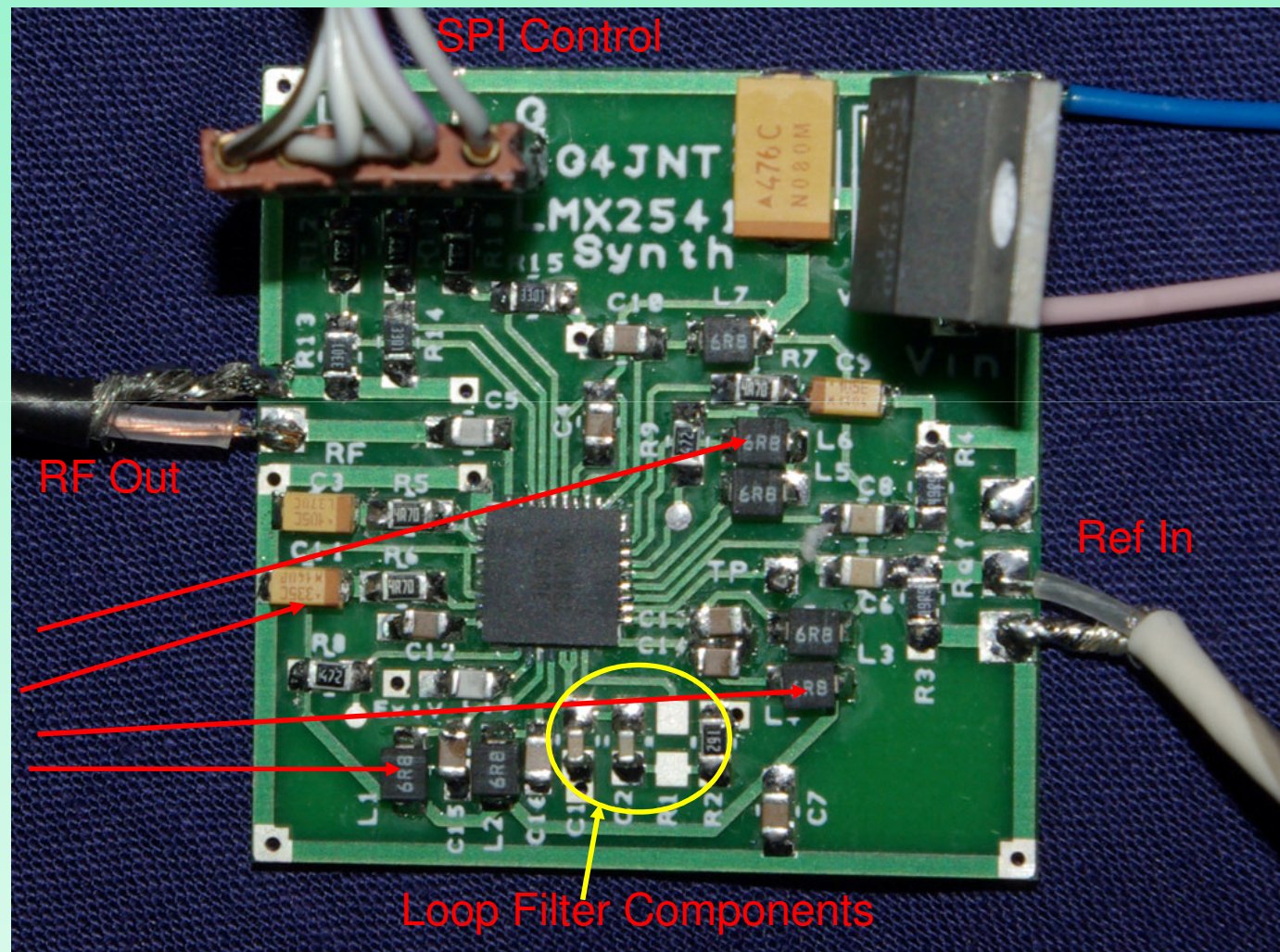

Lots of
Decoupling

But not
much else

RS232 Control

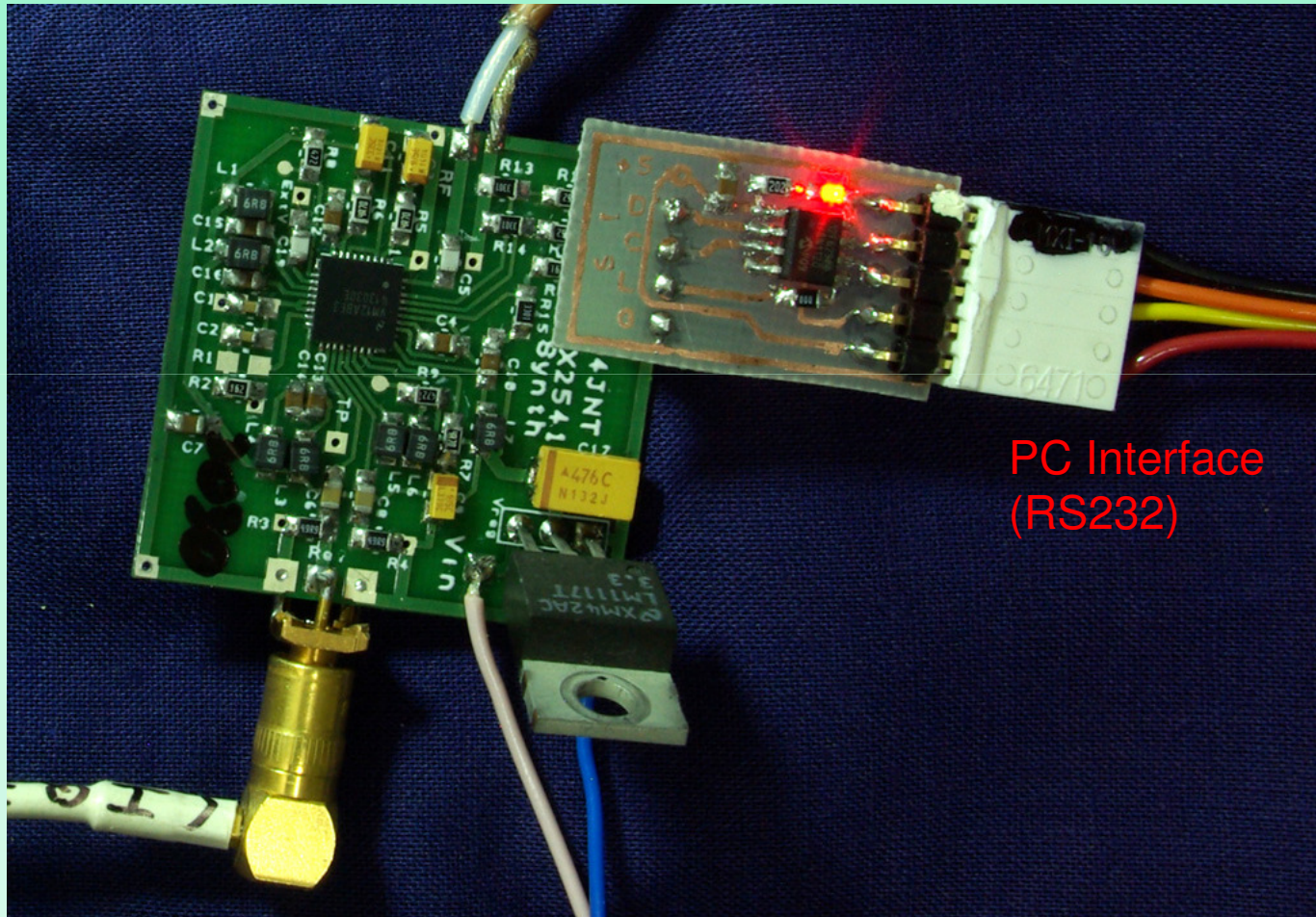

LMX2541 Control G4JNT

Output Freq MHz 432.431 **Fvco** 3459.448 MHz
☒ Fix Fout **Output Divider 8**
☐ Ref Doubler **Chip Version(s) allowed**
LMX2541-3320E

Reference Input MHz 10 **Fcomp** 10000. kHz
R divider 1

Divided O/P Resolution Hz 1 **N = 345**
Step = 8. **MFSK Mode** **F = 1181000**
D = 1250000

Quick Freq Update **Charge Pump Gain** 20 **12 Div Gain**
Update all registers **Strong Dither** **12 VCO Gain**
Store to EE **S-D Modulator** **12 Out Term**
Order 4
Init from EE **Dig Lock Det**
☐ Ext VCO

PIC Register Export

COM 1

7	00000017	13	000000CD
12	0000001C	9	28001409
8	0111CE58	6	001F3326
5	A0040005	4	FF4880A4
3	01487303	2	05312D02
1	04800011	0	05481590


PIC Cut-and-paste

```

; Fout 432.431MHz Resolution 1Hz
; R = 1 D = 1250000 N = 345 F = 1181000
de 0x00, 0x00, 0x00, 0x17 ; Reg7
de 0x00, 0x00, 0x00, 0xCD ; Reg13
de 0x00, 0x00, 0x00, 0x1C ; Reg12
de 0x28, 0x00, 0x14, 0x09 ; Reg9
de 0x01, 0x11, 0xCE, 0x58 ; Reg8
de 0x00, 0x1F, 0x33, 0x26 ; Reg6
de 0xA0, 0x04, 0x00, 0x05 ; Reg5
de 0xFF, 0x48, 0x80, 0xA4 ; Reg4
de 0x01, 0x48, 0x73, 0x03 ; Reg3
de 0x05, 0x31, 0x2D, 0x02 ; Reg2
de 0x04, 0x80, 0x00, 0x11 ; Reg1
de 0x05, 0x48, 0x15, 0x90 ; Reg0

```

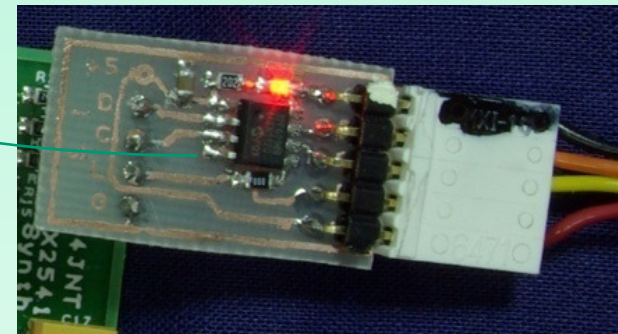Software calculates register contents, then can send RS232 data and stores in the PIC for boot up.



Rotary Control / LCD

